

# 25 KV Power Supply for 1/2MV Marx Construction Notes

2 Mar 11

By Vaughn P. McDowell

Several years ago I was using my handy general purpose ten year old variable HV power supply to power up my 300KV mini-Marx generators. To free it up for other experiments a dedicated 20KV HVPS was constructed specific to these mini-Marx. Later on a 1/2 MV mini Marx was constructed requiring a 25KV HV power supply; based on the 20KV HVPS mentioned above I decided to build a similar unit specific to the new Marx. The original sketch construction operational notes got lost somewhere; the following is an attempt to reverse engineer and document its construction. The output power is about 15 - 20 watts, adequate for my purposes.

The 1/2 MV Marx is shown in the photos below at the left; the top right photo shows the Marx in action producing 18 inch bolts. The 25 KV HVPS is shown in this photo and the one below it.

1/2 MV Marx \ 18 INCH BOLTS

1/2 MV Marx



25KV HVPS

Expanded View




# Some General Comments About This Unit


There are some power up issues that I hope to address in the near future; specifically when the unit is enabled during power up even while the HV output is not loaded. For example, sometimes when first powered up the unit often operates smoothly to its regulated voltage drawing little input rush current; other times the unit draws 4 or more amps overloading the 12VDC power supply rated for only a few amps until the power is interrupted; the applied voltage is pulled down 10 volts or less. This happens in spite of having one of the two sets of TL494 inputs used for current limit sensing. On the other hand if the 12 volt source supplies adequate current (ie car battery) the in rush current is momentary; after which it operates in it normal mode. If the unit is enabled after having been powered up, the unit operates smoothly drawing little input rush current. As long as proper precautions are taken the unit is quite functional; however it is obvious that there are some design issues that need to be worked out.

When operating the 1/2 MV Marx the HVPS was powered up in the enable mode using a 12 volt car battery. In this manner the 25KV power supply operated very satisfactory.




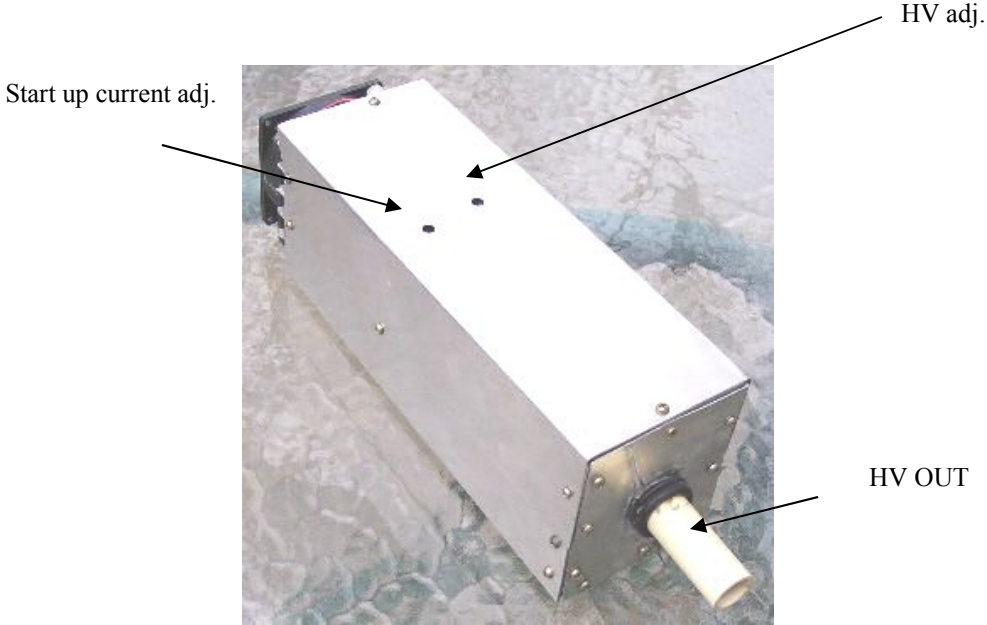
## Construction Note Photos (25KV HVPS) \ angled and rear view




### REAR VIEW

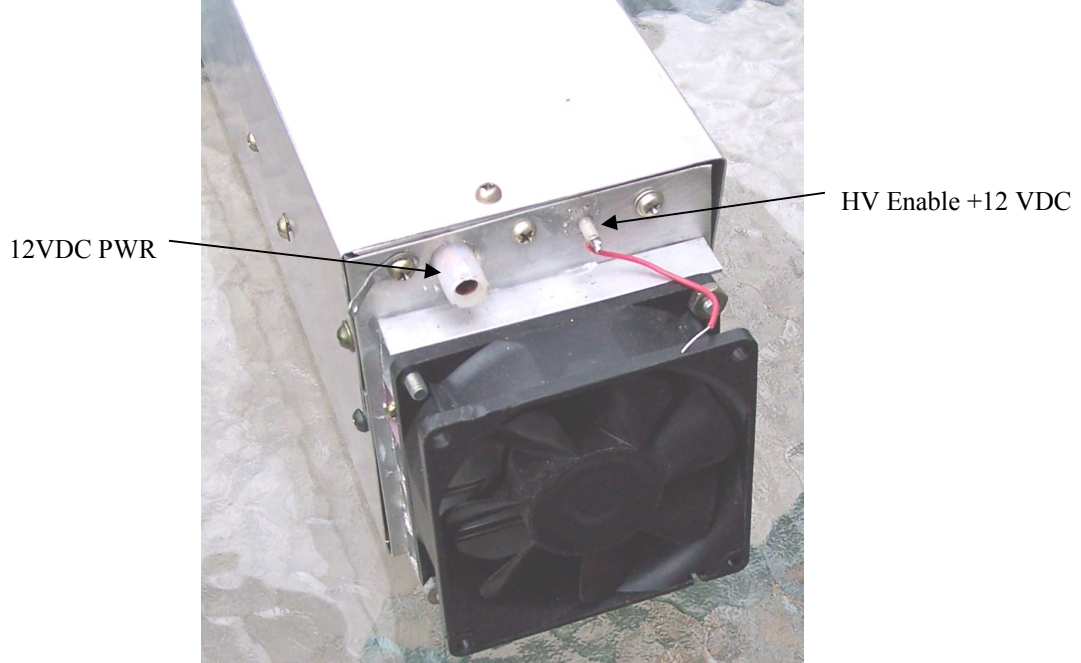
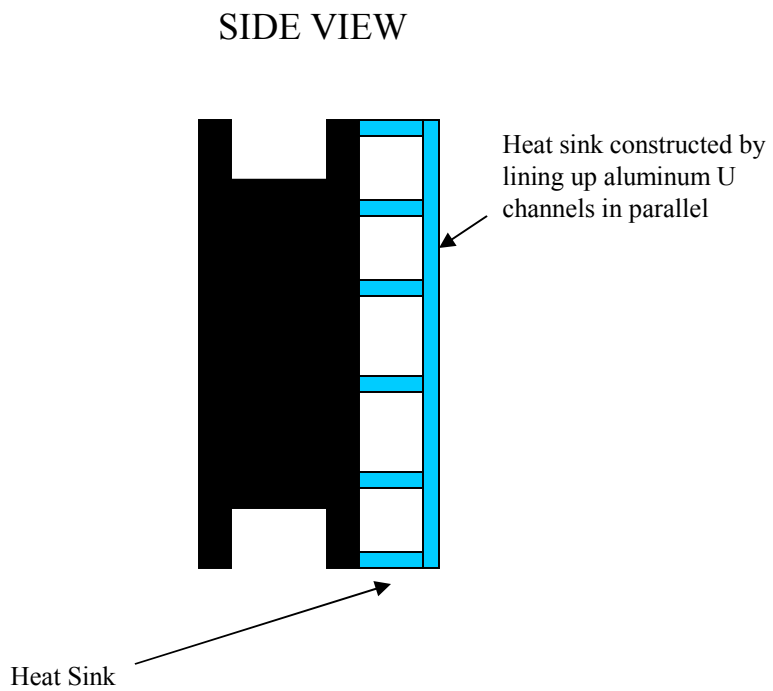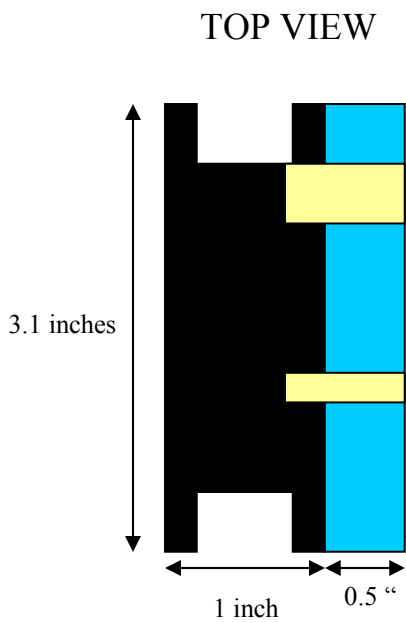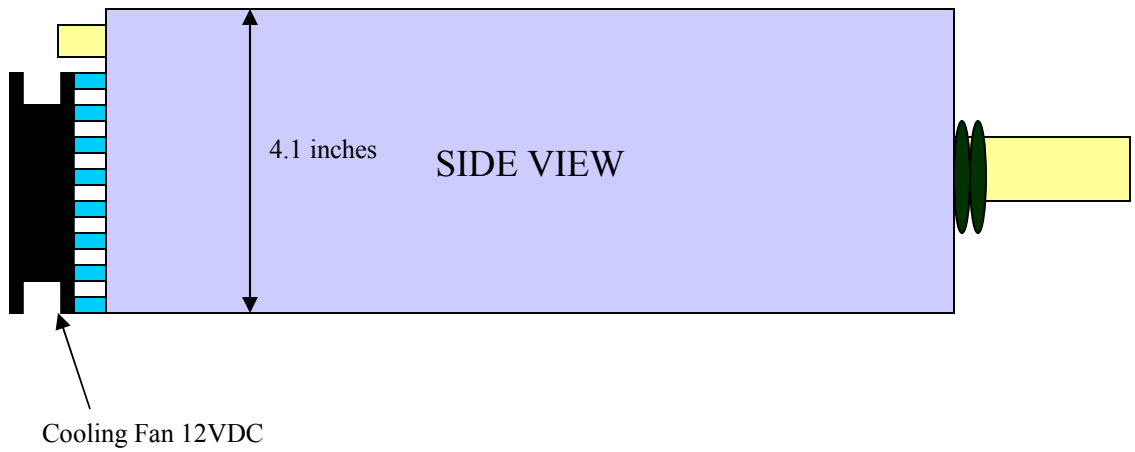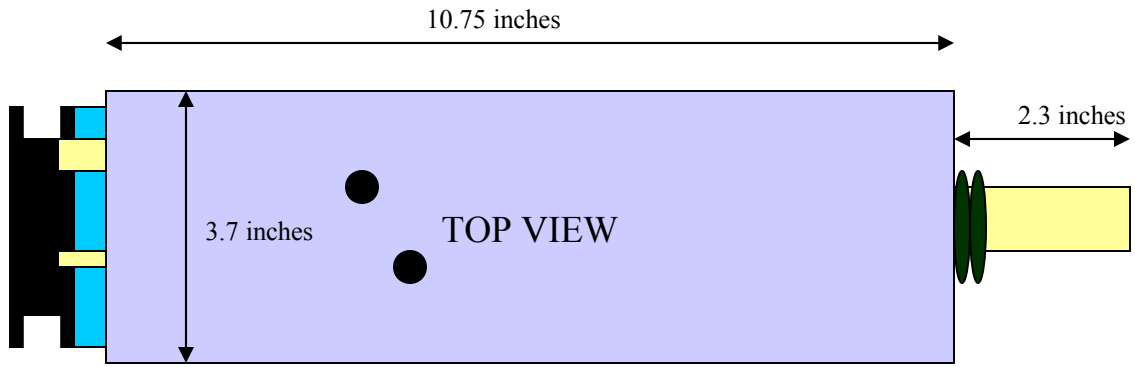
# Construction Note 25KV HVPS UNIT \ Some Physical Outside Dimensions



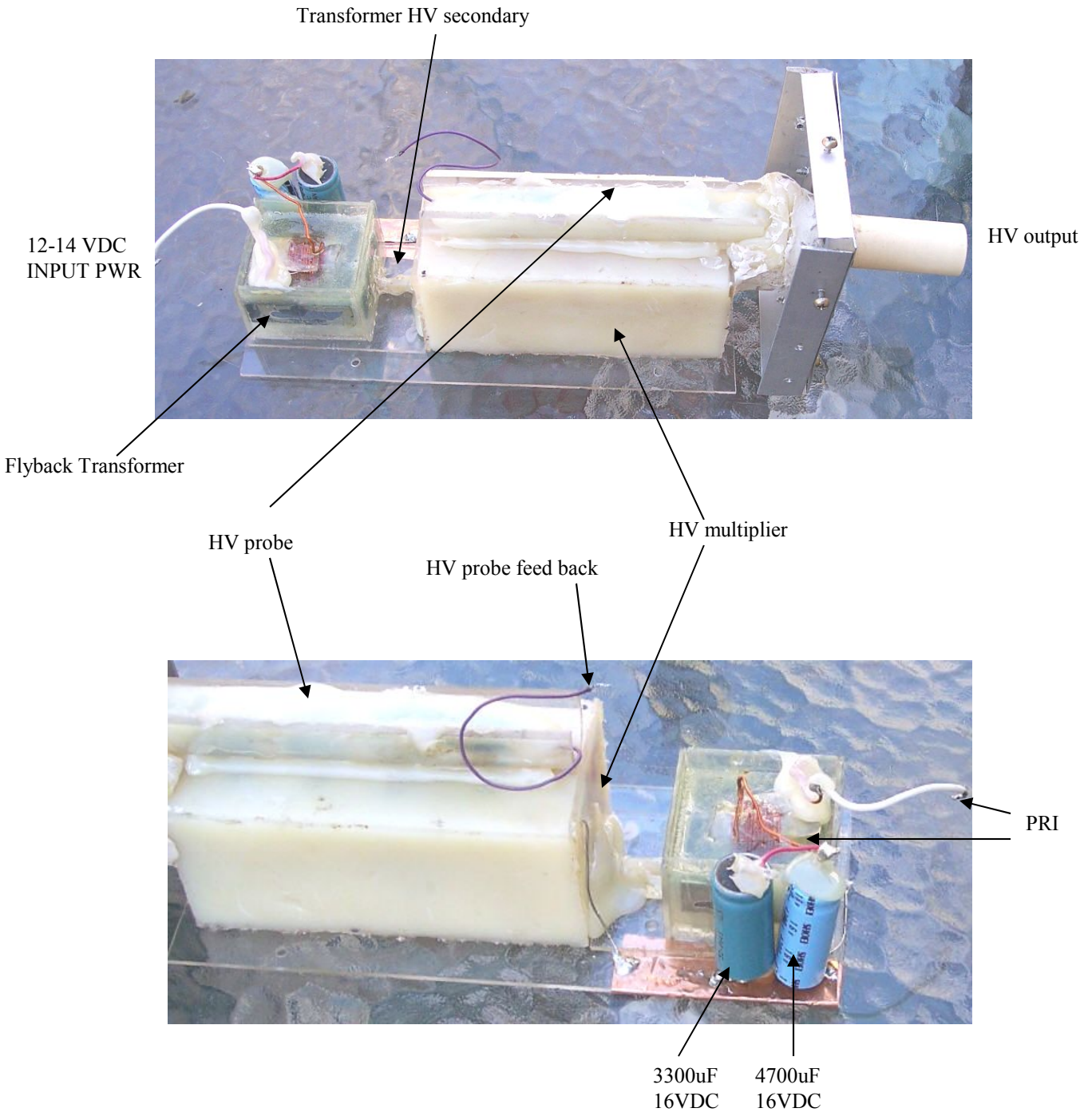
# Construction Note Photos (Quick Overview) \ HV section \ Electronics





# Construction Note Photos (Quick Overview) \ HV section \ Some Physical Dimensions

## TOP VIEW


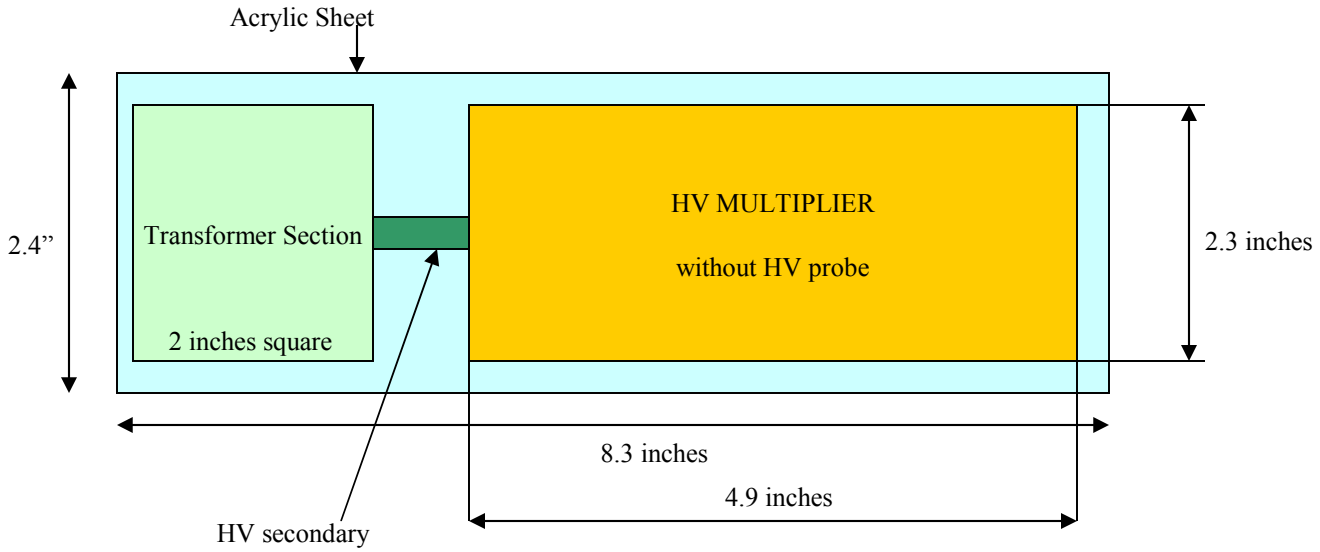


## SIDE VIEW

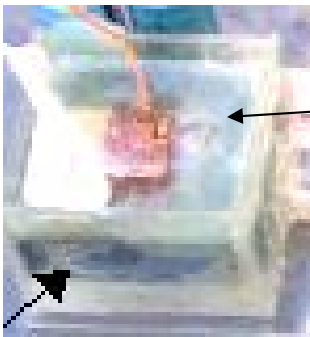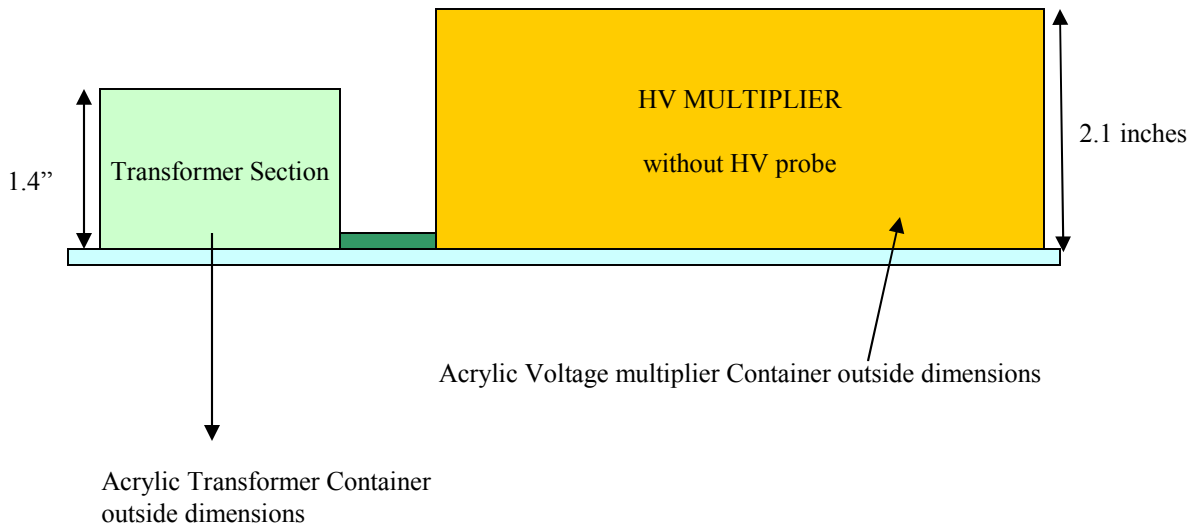


Transformer is inserted in the container which is then filled with epoxy
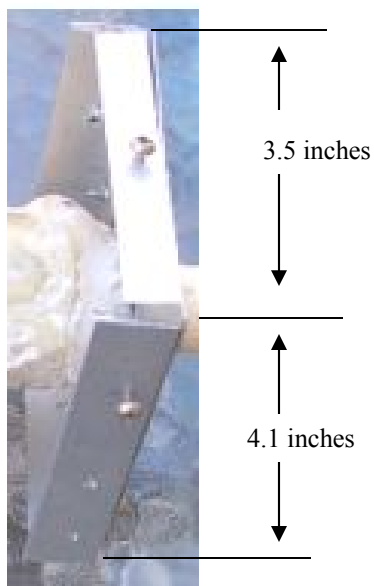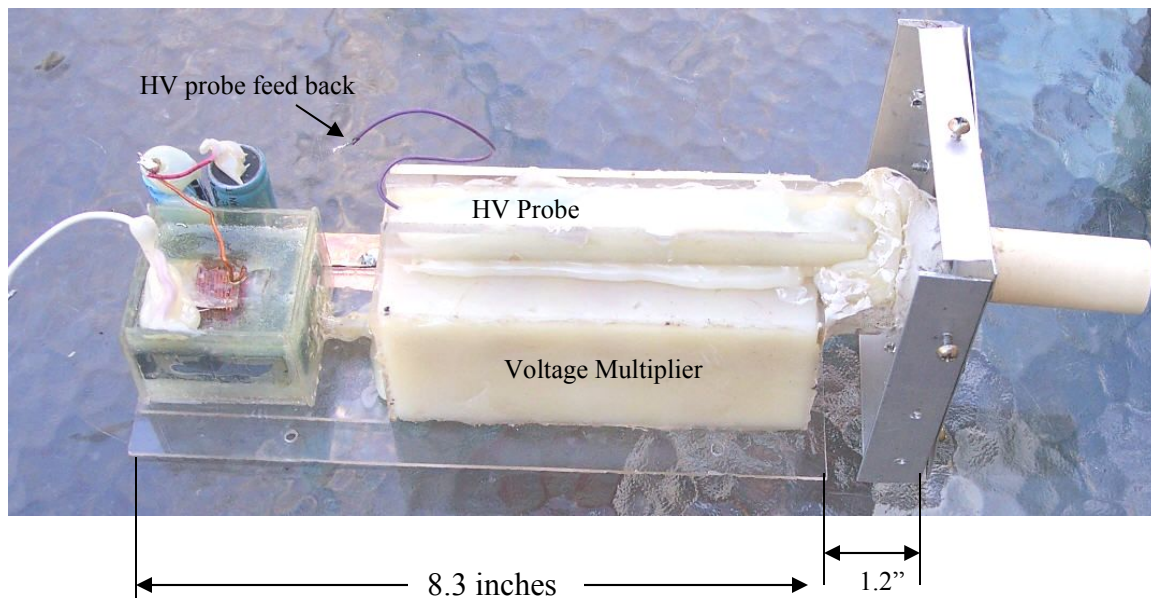
# Construction Note Photos (Quick Overview) \ HV section \ Some Physical Dimensions




# Construction Note Photos (Quick Overview) \ HV section \ Mounted to Metal Case

Side View

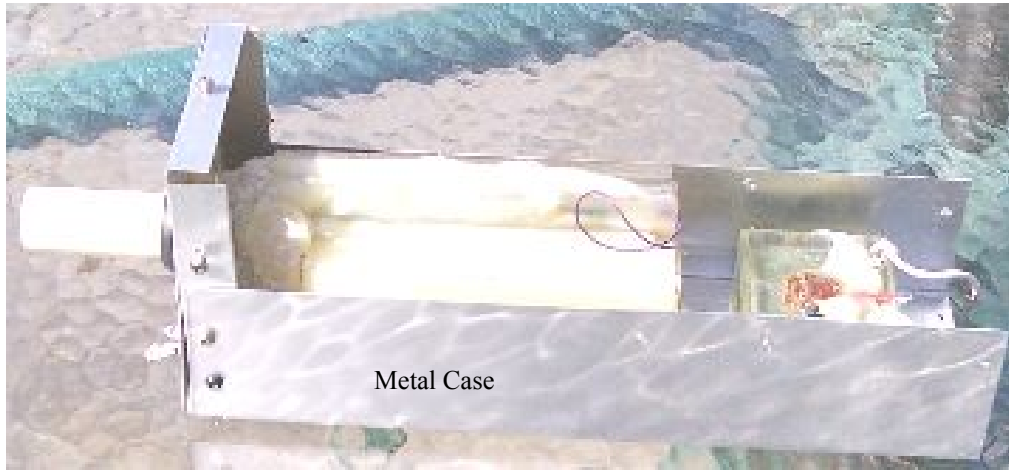


Top View

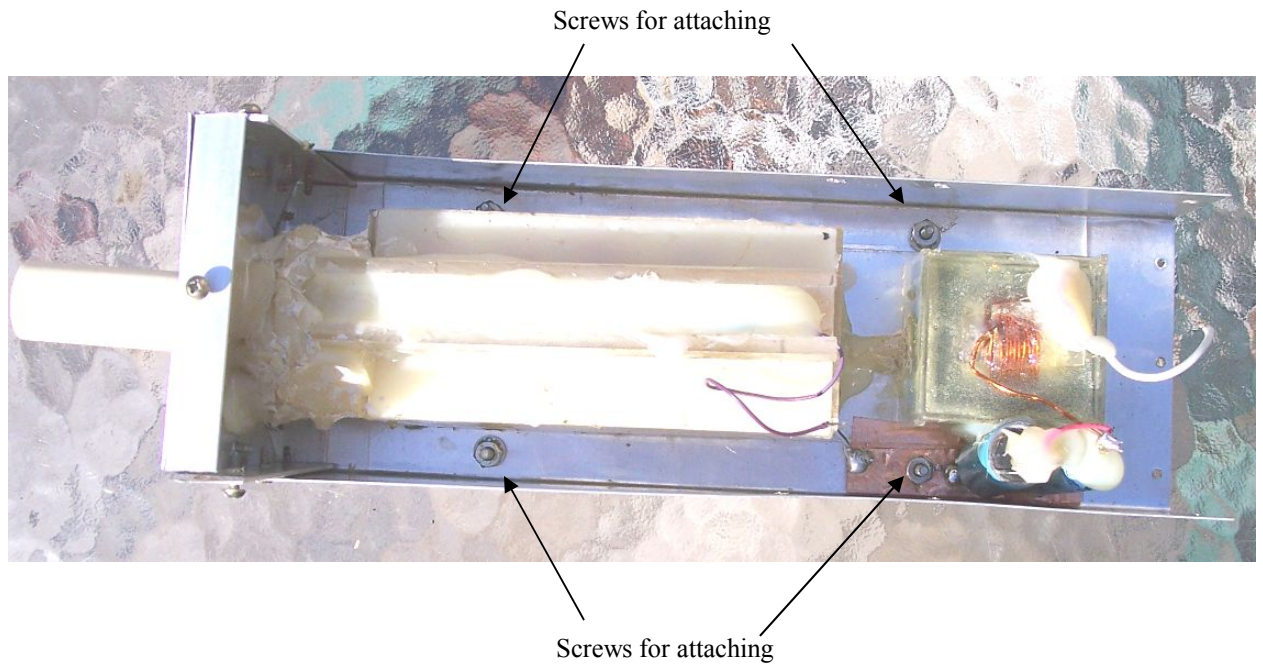

Construction Note Photos (Quick Overview) \ Controller Circuit \ Mounted to Metal Case


Controller circuit

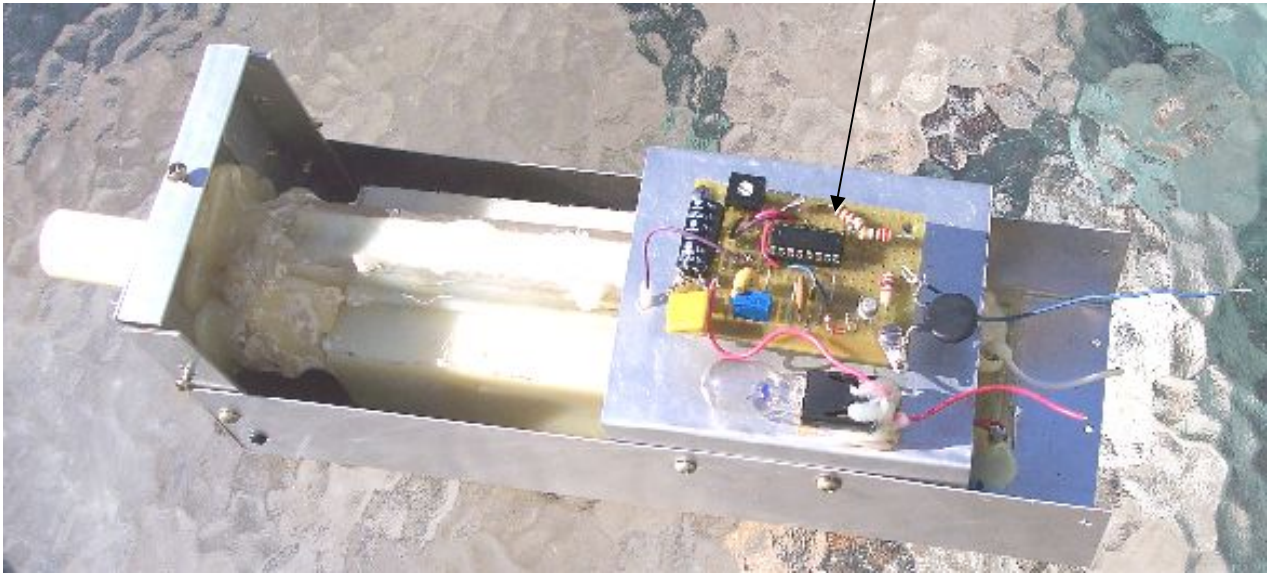

COMPLETED UNIT / Lid Removed


IGBT Section

HV probe feed back

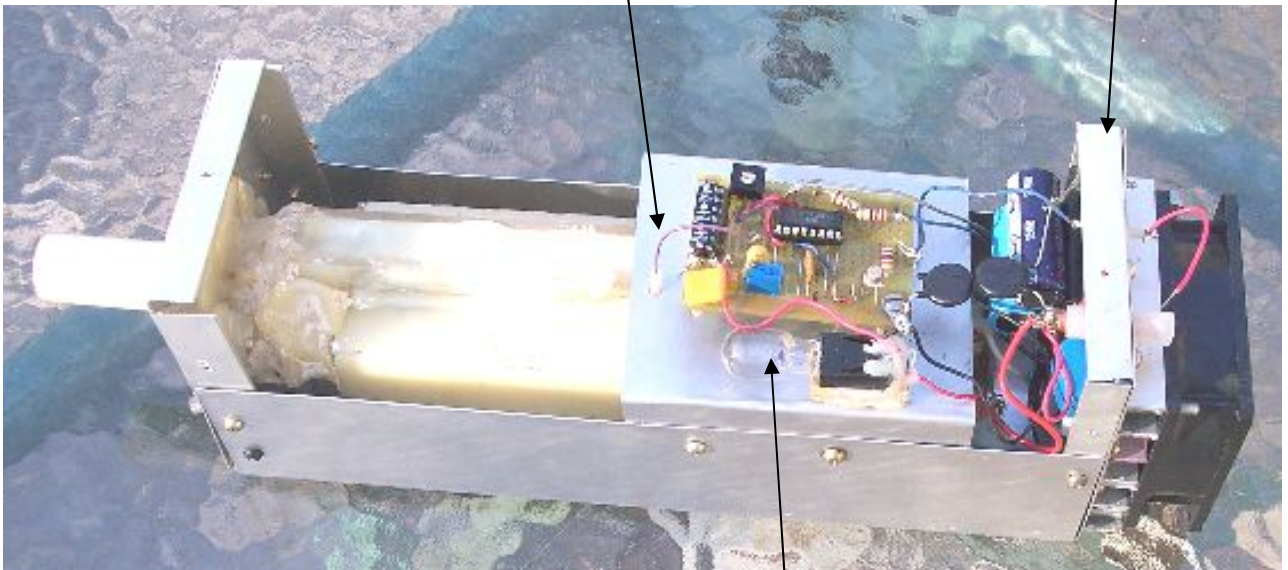

Light bulb current ballast



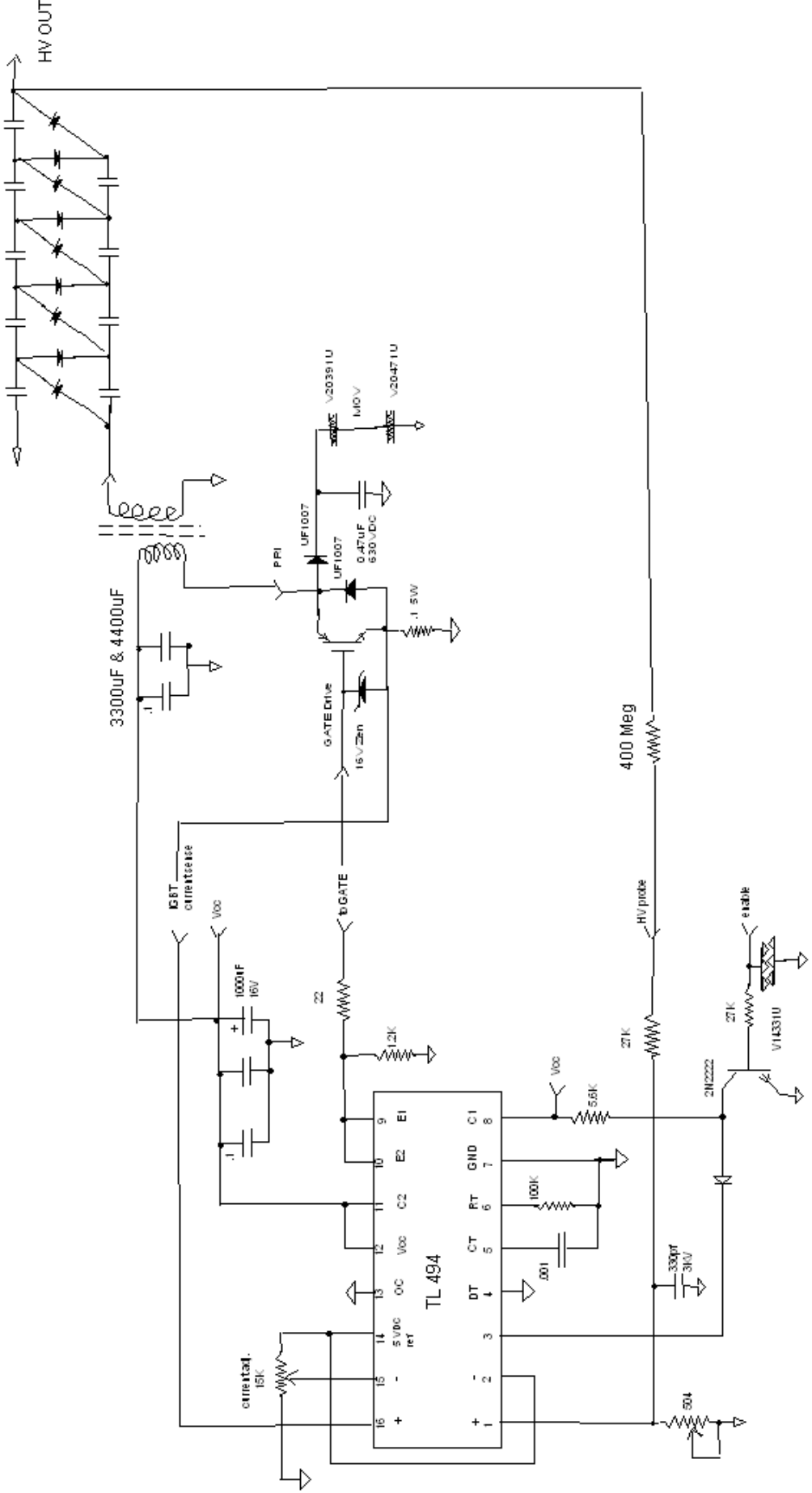

# Construction Note Details \ Controller Circuit



## Comments:

The gate drive source and sink is enhanced by paralleling E1 & 2 and C1 & 2 (emitter and collector). The gate capacitance has the tendency to increase the rise time; the temptation is to connect the gate directly to the drive source. I have learned the hard way that when the IGBT fails the gate seems to short out which in turn shorts the 494 drive. For this reason a gate current limited resistor (22 ohms ) is used. A 1.2K resistor keeps the gate voltage close to zero when the IC is removed for diagnostic purposes.

A third input control was added to pin 3 for the enable circuitry (1N4148, 2N2222, ..). The first input is for voltage adjustment, the second for limiting the current.

This circuit needs design improvements; mostly to address the start up power draw instabilities. Automatic enable after power up etc..


Start up current adj.

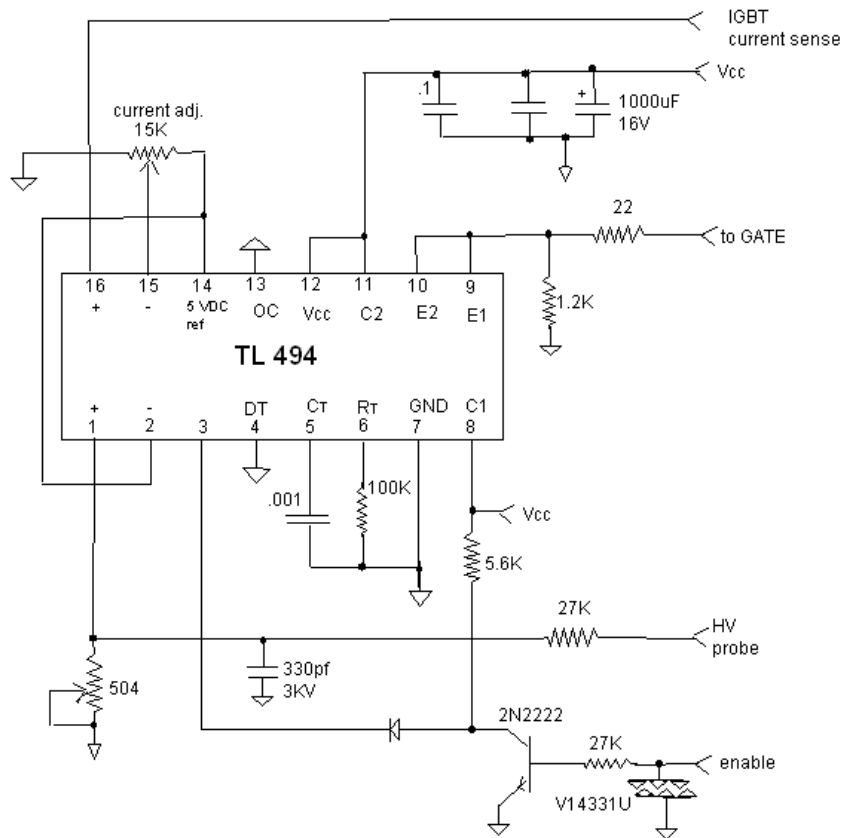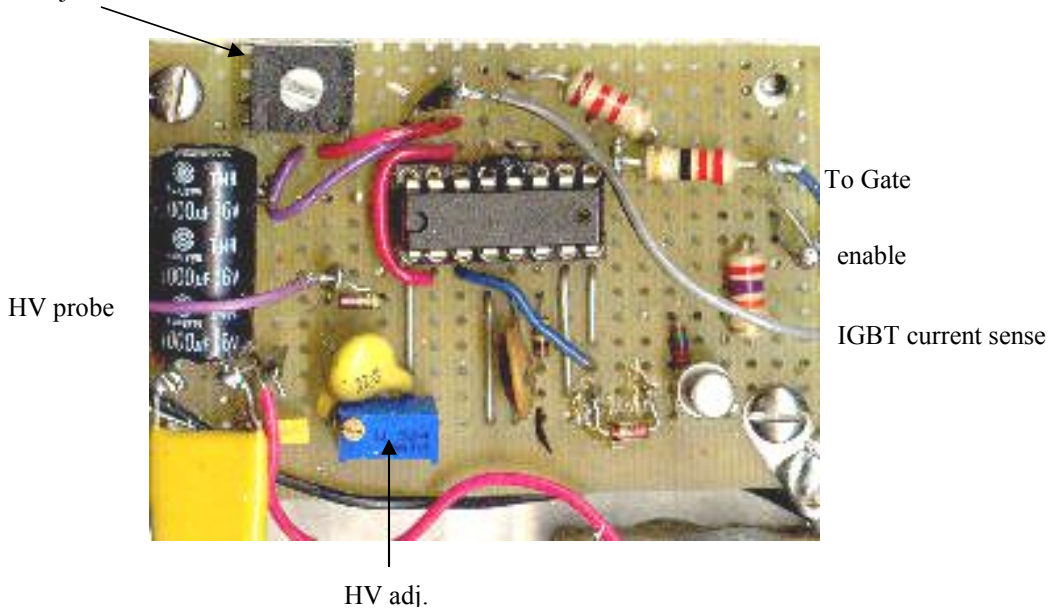

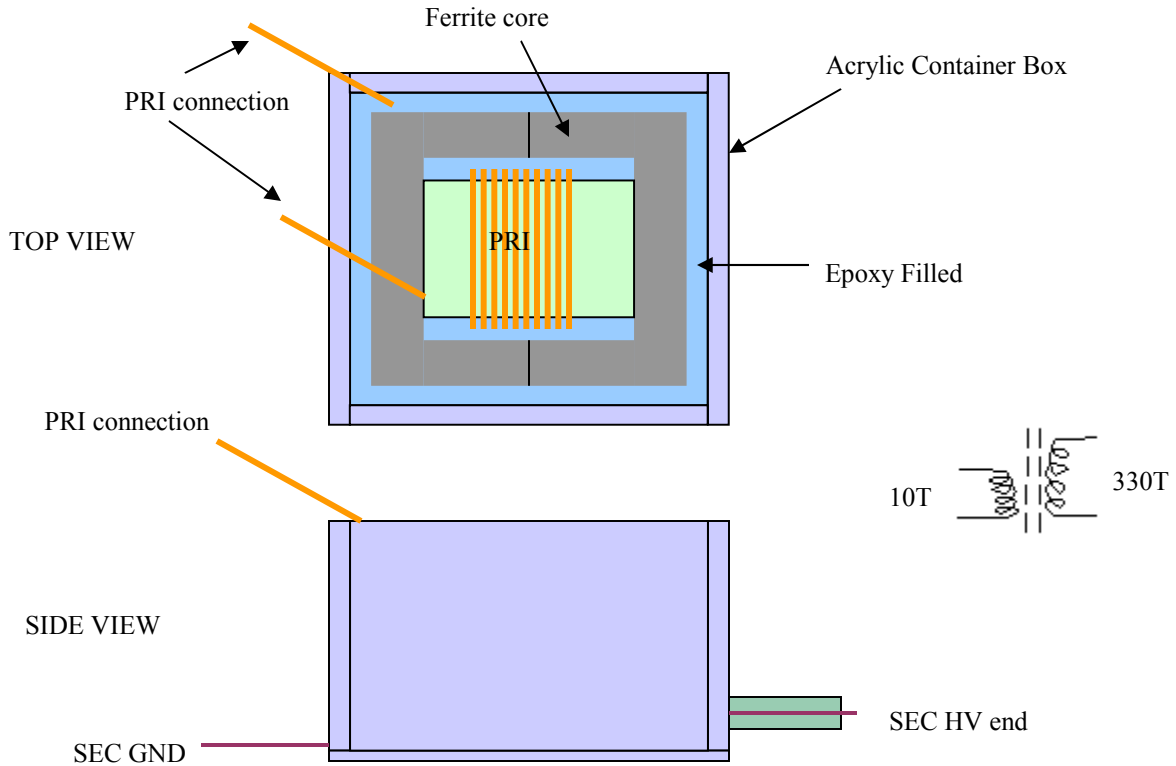
# Construction Note Details \ Transformer

The technique for the flyback transformer construction is described at:  
([http://vaughns\\_page.50webs.com/HV/transformer/flybk\\_A/flybk\\_a.html](http://vaughns_page.50webs.com/HV/transformer/flybk_A/flybk_a.html) )

This project used, when convenient, pre-constructed components; this particular transformer assembly was constructed about two years before this project was conceived. The Fair-Rite core type is believed to be 77; the core itself is ETD part # 9577440002. The primary is 10 T of # 20 magnet wire; the secondary about 330 T # 30 magnet wire.





# Construction Note Details \ HV Probe

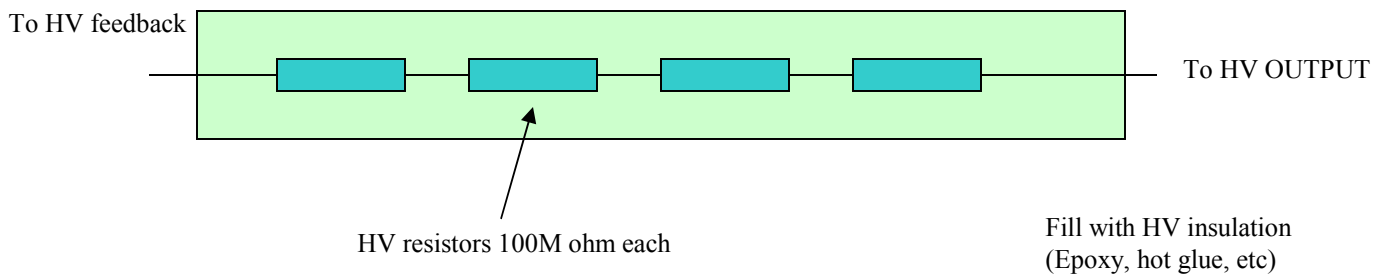
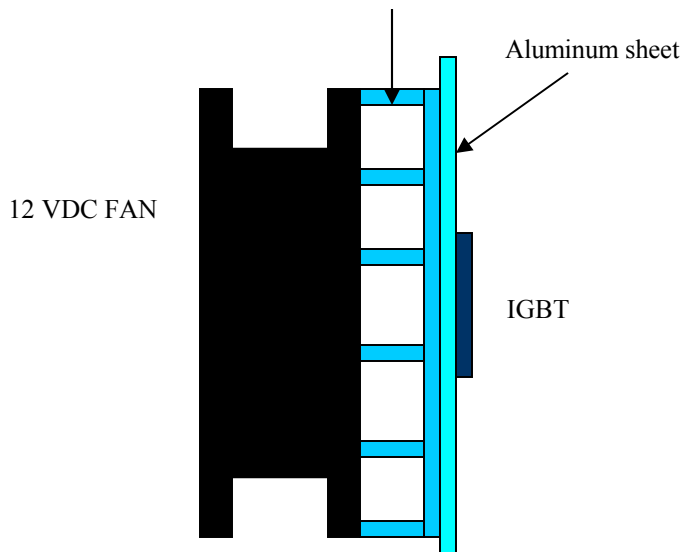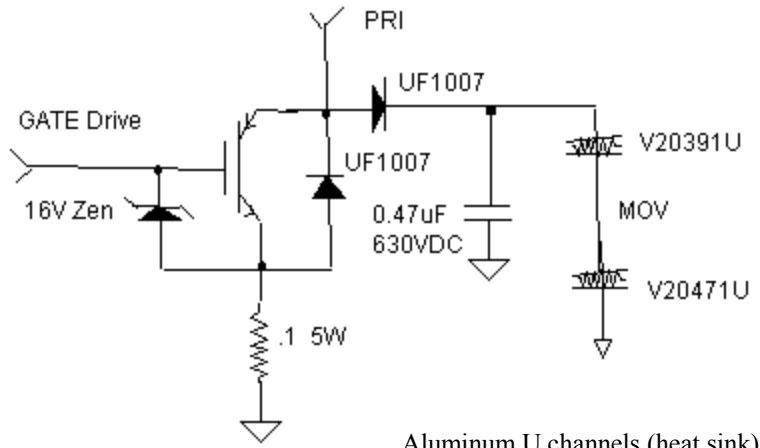
# Construction Note Details \ IGBT Section


The IGBT section is a circuit I used ten years ago on a flyback transformer project; the IGBT is of the 1200 Volt type IRG4PH50U or similar; the diodes are of the ultra fast recovery UF1007. The remaining components protect the GATE ( 16 volt Zenor) and anode (MOVs etc.)



# Construction Note Details \ HV Multiplier Section

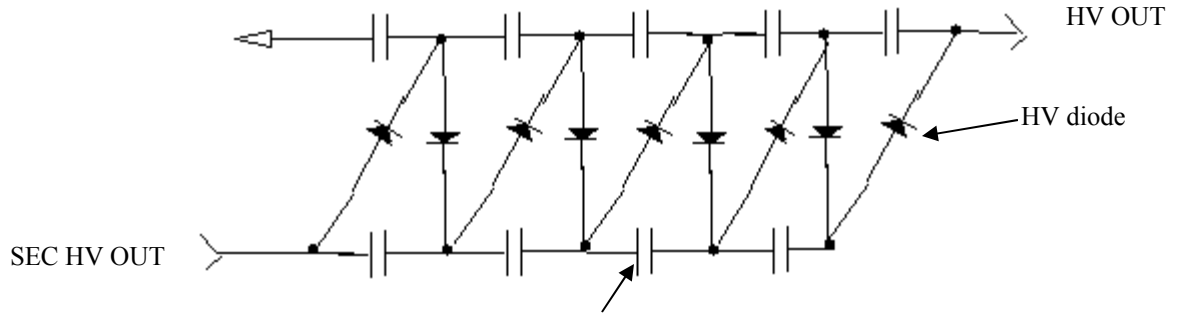
## Comments:

The voltage multiplier was constructed some time ago and shelved; most of the components are not visible being immersed in HV insulation (epoxy and hot glue). The circuit diagram shown below ( for documentation purposes) is my best guess even though it doesn't represent the type I normally use;




Each capacitor : CERAMITE 2.5nF 15 KV

SIDE A VIEW

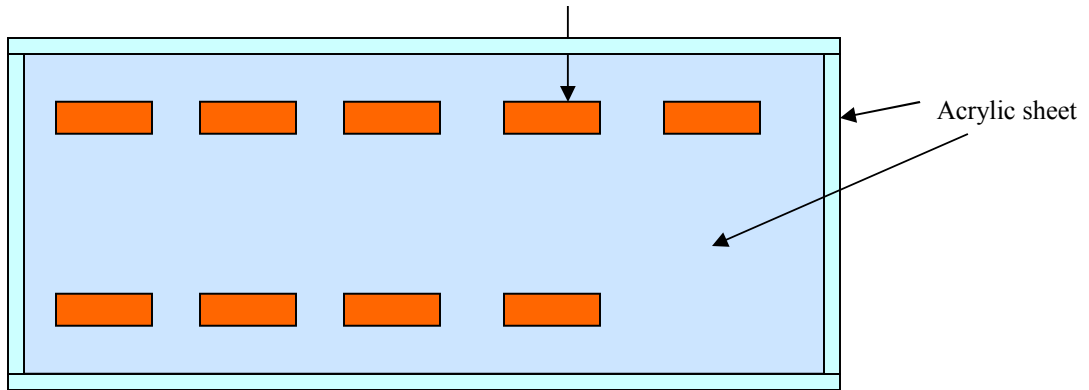

Fill Acrylic enclosure with HV insulation


SIDE B VIEW

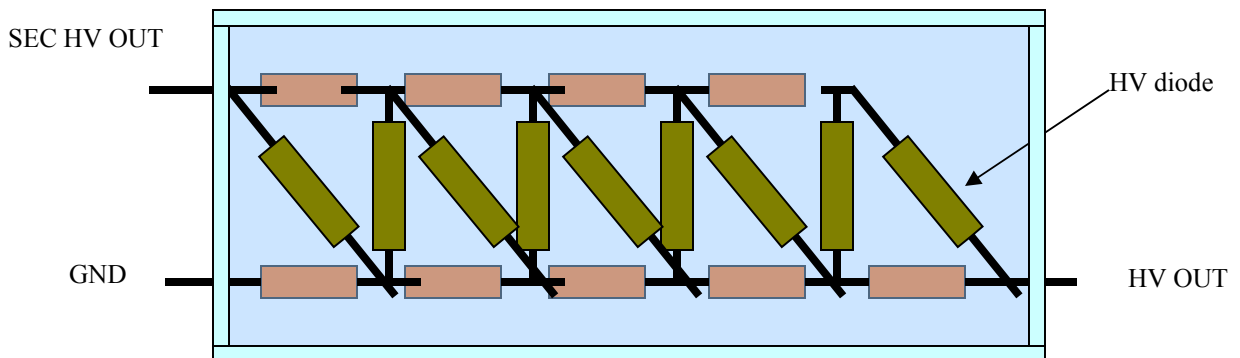


# Construction Note Details \ HV Multiplier Section \ HV Diodes
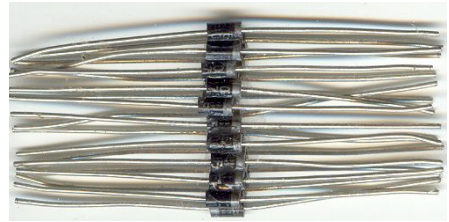
## HV Diode Construction


Ultra fast diode type UF1007 1KV PIV @ 1A (Digi-Key) are laid out parallel in groups of tens super glued together. After drying two of the ten glued diode sections are stacked and glued. Take careful note below of the orientation of the anode and cathode. These twenty diodes are to be connected and soldered in series. When carefully assembled I have had very good success with these.



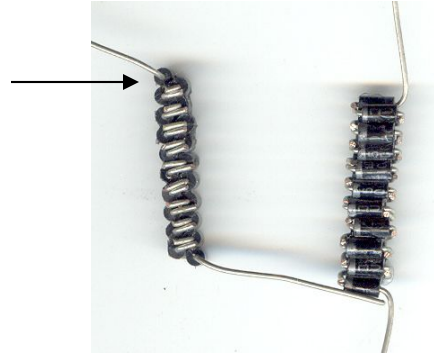After the two layers are glued the leads are trimmed to length except for the end sections



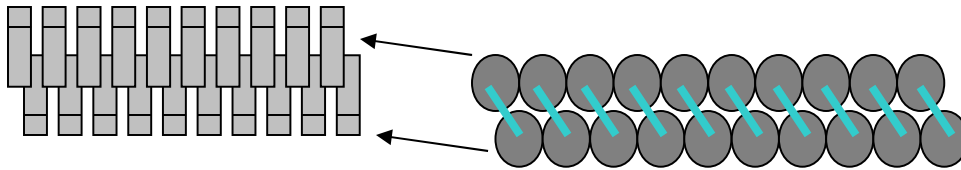The folded and trimmed leads are carefully soldered together; keep solder smooth as possible to reduce HV stress



The soldered diode assembly is cleaned(alcohol) and dried; then carefully given an epoxy coating being careful to work out any air bubbles between the soldered leads

## Construction Note Details \ HV Multiplier Section \ HV Probe

